



IC OVERVIEW

RTL DESIGN AND VERIFICATION

COURSE INTRODUCTION

Khóa Học Thiết Kế Vi Mạch Cơ Bản - Trung Tâm Đào Tạo Thiết Kế Vi Mạch ICTC



KHÓA THIẾT KẾ VI MẠCH CƠ BẢN

Khóa học đào tạo cho các bạn các kiến thức kỹ năng cơ bản về vi mạch, chú trọng thực hành thiết kế và kiểm tra mạch để tạo nền tảng vững chắc cho sự nghiệp vi mạch sau này!

LỘ TRÌNH TỰ HỌC VI MẠCH 📖

KHÓA HỌC THIẾT KẾ VI MẠCH 🎓

- ✓ Giảng viên là các kỹ sư vi mạch hơn 5 - 10 năm trong nghề
- ✓ Giáo trình hiện đại đúc kết từ các công ty vi mạch toàn cầu
- ✓ Tập trung đào tạo thực hành về kỹ năng cần thiết khi làm kỹ sư vi mạch
- ✓ Phần mềm học trực tiếp trên Server đang được các công ty sử dụng
- ✓ Kinh nghiệm, kiến thức về tìm việc làm, phỏng vấn ngành vi mạch

COURSE INTRODUCTION



SUMMARY



HOMEWORK



QUESTION



SELF-LEARNING

Session 3: Optimize Boolean Functions and Introduction To Combinational and Sequential Circuits



1. K-map
2. Combinational Circuit
3. Sequential Circuit

LOGIC GATE

KARNAUGH MAP



Karnaugh map it is a graphical representation of a truth table for a Boolean function. Karnaugh maps are helpful for simplifying Boolean expressions and minimizing the number of terms in a logic function.

ICTC TRAINING CENTER

LOGIC GATE

KARNAUGH MAP – 2 VARIABLES



K-map to represent $F(A,B)$ - SOP

A	B	minterms	
0	0	$\bar{A}\bar{B}$	m0
0	1	$\bar{A}B$	m1
1	0	$A\bar{B}$	m2
1	1	AB	m3

	\overline{B}	B
\overline{A}	$\overline{A} \overline{B}$	$\overline{A} B$
A	$A \overline{B}$	AB

	B	0	1
A		m0	m1
	0		
	1	m2	m3

LOGIC GATE

KARNAUGH MAP – 2 VARIABLES



Optimize K-map rules:

- ☐ Make the group of 1s, which are adjacent to each other.
- ☐ This group should be in the power of 2. For example, in case of the 2 variables map, we can make the group of two 1s or group of four 1s, but can not make the group of three 1s.
- ☐ Ensure that during the grouping, all the 1s in the maps are covered.
- ☐ During grouping, even if the 2 groups overlap with each other, it's alright.
- ☐ After grouping, keep the common variables (not change) in each group.

LOGIC GATE

KARNAUGH MAP – 2 VARIABLES GROUPING

A \ B	0	1
0	1	1
1		1

A \ B	0	1
0	1	1
1	1	1

A \ B	0	1
0	1	1
1		1



LOGIC GATE

KARNAUGH MAP – 2 VARIABLES

$$F(A,B) = A'.B' + A'.B + A.B$$

A	B	F
0	0	1
0	1	1
1	0	0
1	1	1

B	0	1
A	1	1
1		1

$$F(A,B) = A' + B$$

$$F(A,B) = A'.B + A.B'$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

	0	1
A		1
1	1	

$$F(A,B) = A'.B + A.B'$$

Can not be simplified !!!



LOGIC GATE

KARNAUGH MAP – 3 VARIABLES



K-map to represent $F(A,B,C)$ - SOP

A	B	C	minterms
0	0	0	m0
0	0	1	m1
0	1	0	m2
0	1	1	m3
1	0	0	m4
1	0	1	m5
1	1	0	m6
1	1	1	m7

A \ BC	00	01	11	10
0	m0 →	m1 →	m3 ←	m2 ←
1	m4 →	m5 →	m7 ←	m6 ←

LOGIC GATE

KARNAUGH MAP – 3 VARIABLES

Simplify below Boolean function: $F(A,B,C) = \sum(0,1,3,5)$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

A \ BC	00	01	11	10
0	m0	m1	m3	m2
1	m4	m5	m7	m6

A \ BC	00	01	11	10
0	1	1	1	
1		1		

$$F(A,B,C) = A'.B' + A'.C + B'.C$$



LOGIC GATE

KARNAUGH MAP – 3 VARIABLES - GROUPING

$$F(A,B,C) = \sum(0,2)$$

A \ BC	00	01	11	10
0	1			1
1				

$$F(A,B,C) = \sum(4,6)$$

A \ BC	00	01	11	10
0				
1	1			1

$$F(A,B,C) = \sum(1,3,5,7)$$

A \ BC	00	01	11	10
0		1	1	
1		1	1	

$$F(A,B,C) = \sum(0,2,4,6)$$

A \ BC	00	01	11	10
0	1			1
1	1			1



LOGIC GATE

KARNAUGH MAP – 3 VARIABLES

Practice: simplify below Boolean function



$$F(A,B,C) = \sum(0,1,2,4,5,6)$$

A \ BC	00	01	11	10
0				
1				

F(A,B,C)=

$$F(A,B,C) = \sum(0,1,2,3,4,6)$$

A \ BC	00	01	11	10
0				
1				

F(A,B,C)=

LOGIC GATE

KARNAUGH MAP – 3 VARIABLES

When the SOP Boolean functions is not enough (lack of variables to form a minterm).

For example:

$$F(A,B,C) = A' + A.B' + A.B.C'$$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

A \ BC	00	01	11	10
0	m0	m1	m3	m2
1	m4	m5	m7	m6

A \ BC	00	01	11	10
0	1	1	1	1
1	1	1		1

$$F(A,B,C)=$$



LOGIC GATE

KARNAUGH MAP – 3 VARIABLES

When the SOP Boolean functions is not enough (lack of variables to form a minterm).

For example:

$$F(A,B,C) = A' + A.B' + A.B.C'$$

A	B	C	minterms
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	

A \ BC	00	01	11	10
0	m0	m1	m3	m2
1	m4	m5	m7	m6

A \ BC	00	01	11	10
0	1	1	1	1
1	1	1		1

$$F(A,B,C) = A' + B' + C'$$



LOGIC GATE

HOMEWORK

Homework1:

- As we already used K-map to simplified the expression in above example.
Let's use Boolean Algebra to prove that:

$$F(A,B,C) = A' + A.B' + A.B.C' = A' + B' + C'$$



LOGIC GATE

KARNAUGH MAP – 4 VARIABLES

K-map to represent $F(A,B,C,D)$ - SOP

A	B	C	D	minterms
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15

CD \ AB	00	01	11	10
00	m0 →	m1 →	m3 ←	m2 ←
01	m4 →	m5 →	m7 ←	m6 ←
11	m12 →	m13 →	m15 ←	m14 ←
10	m8 →	m9 →	m11 ←	m10 ←



LOGIC GATE

KARNAUGH MAP – 4 VARIABLES - GROUPING

Grouping of 4 and 8, as long as the 1s are adjacent

CD \ AB	00	01	11	10
00	1	1	1	1
01		1	1	
11		1	1	
10	1			1

Groupings in the first Karnaugh map:

- A green dashed rectangle groups the four 1s in the top row (CD=00).
- A blue dashed rectangle groups the four 1s in the middle two rows (AB=01 and AB=11).
- Red dashed lines indicate wrap-around groupings: a horizontal group for the first and last columns (AB=00 and AB=10) in the top and bottom rows, and a vertical group for the first and last columns (CD=00 and CD=10) in the top and bottom rows.

CD \ AB	00	01	11	10
00	1	1	1	1
01		1	1	
11		1	1	
10	1	1	1	1

Groupings in the second Karnaugh map:

- A blue dashed rectangle groups the four 1s in the middle two columns (CD=01 and CD=11).
- Yellow dashed lines indicate wrap-around groupings: a horizontal group for the first and last columns (AB=00 and AB=10) in the top and bottom rows, and a vertical group for the first and last columns (CD=00 and CD=10) in the top and bottom rows.

LOGIC GATE

KARNAUGH MAP – 4 VARIABLES

$$F(A,B,C,D) = \sum(0,2,5,9,10)$$

CD \ AB	00	01	11	10
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

CD \ AB	00	01	11	10
00	1			1
01		1		
11				
10		1		1



LOGIC GATE

KARNAUGH MAP – 4 VARIABLES

$$F(A,B,C,D) = \sum(0,2,5,9,10)$$

CD \ AB	00	01	11	10
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

CD \ AB	00	01	11	10
00	1			1
01		1		
11				
10		1		1

$$F(A,B,C,D) = A'.B'.D' + A'.B.C'.D + A.B'.C'.D + B'.C.D'$$

LOGIC GATE

KARNAUGH MAP – 4 VARIABLES

$$F(A,B,C,D) = \sum(4,5,6,7,9,13,14,15)$$



CD \ AB	00	01	11	10
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

CD \ AB	00	01	11	10
00				
01	1	1	1	1
11		1	1	1
10		1		

LOGIC GATE

KARNAUGH MAP – 4 VARIABLES



CD \ AB	00	01	11	10
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

$$F(A,B,C,D) = \sum(4,5,6,7,9,13,14,15)$$

CD \ AB	00	01	11	10
00				
01	1	1	1	1
11		1	1	1
10		1		

$$F(A,B,C,D) = A'.B + BC + A.C'.D$$

LOGIC GATE

KARNAUGH MAP – 4 VARIABLES

Practice: simplify below $F(A,B,C,D) = \sum(0,1,5,6,7,8,9,13,15)$

CD \ AB	00	01	11	10
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

CD \ AB	00	01	11	10
00				
01				
11				
10				

$F(A,B,C,D) =$



LOGIC GATE

KARNAUGH MAP – 4 VARIABLES

Practice: simplify below $F(A,B,C,D) = \sum(0,1,4,5,7,8,9,11,12,13,15)$

CD \ AB	00	01	11	10
00	m0	m1	m3	m2
01	m4	m5	m7	m6
11	m12	m13	m15	m14
10	m8	m9	m11	m10

CD \ AB	00	01	11	10
00				
01				
11				
10				

$F(A,B,C,D) =$



LOGIC GATE

HOMEWORK

Homework2:


- ☐ A circuit has 4 inputs A,B,C,D and 1 output Y. Design a combinational logic for Y to set Y to 1 whenever 2 or more inputs are equal to 1. Otherwise, Y is 0. Use SOP form.
- ☐ *Investigate 5 variable K-map and do the same requirement as above homework. Use SOP form.



COMBINATIONAL CIRCUIT

Below is some characteristics of combinational circuit:



- ❑ **No feedback:** do not have feedback paths, meaning there are no elements that store information about previous inputs or outputs.
- ❑ **Instantaneous Output:** The output is a function only of the current input values, and there is no concept of time or sequence.
- ❑ **Truth Table:** The behavior of a combinational circuit is fully described by a truth table, which lists all possible combinations of input values and their corresponding output values.
- ❑ **Logic Gates:** Combinational circuits are constructed using basic logic gates such as AND, OR, NOT, XOR, and others.

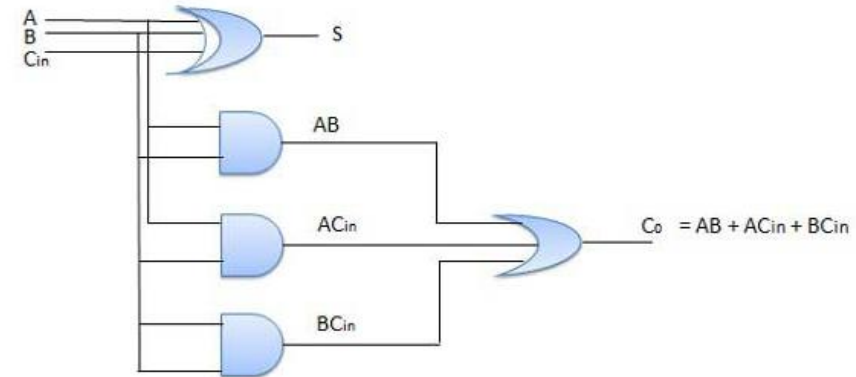

SEQUENTIAL CIRCUIT

Below is some characteristics of combinational circuit:

- ❑ **Memory Elements:** Sequential circuits include memory elements (such as flip-flops or latches) that store information about the past states of the circuit.
- ❑ **Feedback Paths:** Sequential circuits have feedback paths that allow the output to influence the input, creating a loop that enables the circuit to maintain and update its state.
- ❑ **Clock Signal:** The clock signal determines when the circuit should update its state, ensuring that changes happen at specific intervals.
- ❑ **State Transition:** The behavior of a sequential circuit is often described using a state diagram, which illustrates how the circuit transitions from one state to another based on input and clock signals.
- ❑ **Finite State Machines:** Sequential circuits are often implemented as finite state machines, where the circuit can exist in a finite number of states, and transitions between states are governed by specified conditions.

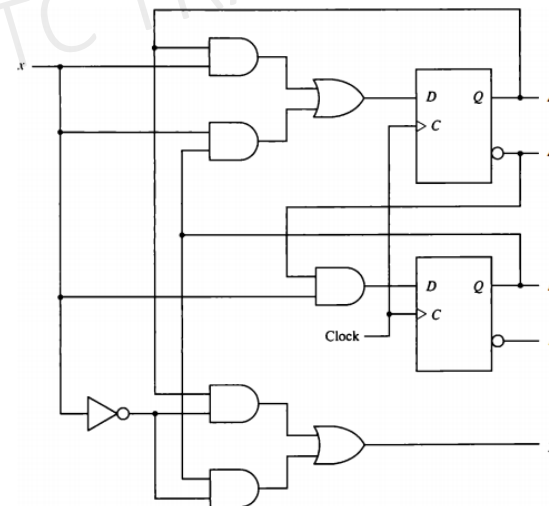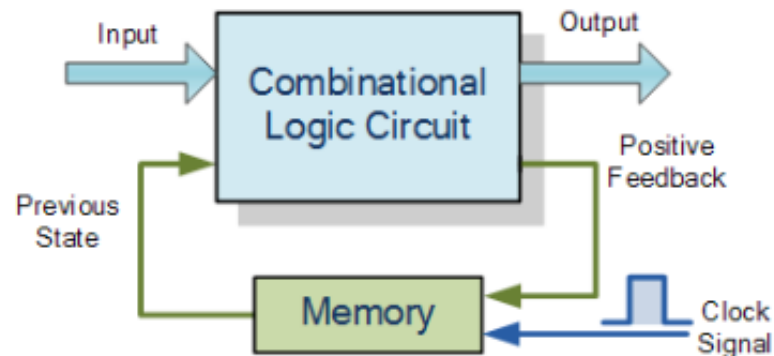

SUMMARY

SUMMARY:

- ❑ Karnaugh map is a very effective way to simplify Boolean functions.
- ❑ Combinational logic has no feedback path, the output changes immediately based on input.
- ❑ Sequential logic has feedback path to store the current state.

